



## Plan Your Circuit

Using the model circuit diagram by Natalie Freed, draw out a circuit that places the LED underneath what you've chosen to illuminate.

Consider placing the microcontroller somewhere it can act as a mechanical switch.

